

ECSE 222, Digital Logic

VHDL 3:

Adders and Critical Path

Fall 2023
University of McGill

Presented by:

Nara Yun (Student #: 261115268)

Karen Chen Lai (Student #: 261107674)

Instructors: Prof. Boris Vaisband

Teaching Assistant: Maninder Bir Singh Gulshan

Date: October 24rd, 2023

Executive Summary

This experiment consists of a few parts with a final purpose of advancing our practice and understanding of digital circuit design by implementing and simulating complex adder circuits. In this assignment, we implemented half adder, full adder, 4-bit Ripple-Carry Adder, one-digit BCD Adder and critical path of digital circuits.

First part consists of the design of a 4-bit Ripple-Carry Adder (RCA). We implemented a structural description of a 4-bit RCA, utilizing basic building blocks like half-adders and full-adders. Then we designed and tested a VHDL structural model for the 4-bit RCA, incorporating thorough testing to ensure functionality. Moreover, we crafted a behavioral VHDL description of the same 4-bit RCA circuit, this time using arithmetic operators. A comprehensive testbench was created for the behavioral description, conducting exhaustive tests to validate its performance.

The second part is the design of a One-Digit Binary Coded Decimal (BCD) Adder. We constructed a structural description for the BCD adder, offering the flexibility to use either structural or behavioral coding styles. A detailed VHDL code was implemented for the structural BCD adder, and extensive testing was performed to validate its functionality. In addition, we devised a behavioral VHDL description for the BCD adder circuit, with a focus on conditional signal assignments. Same as the first part, we constructed a testbench for conducting exhaustive tests for BCD adder descriptions.

The last part is the critical Path Analysis. We learned how to utilize Quartus Timing Analyzer tools to identify the critical path in digital circuits. Timing constraints were introduced to gauge latency, and slack values were determined to evaluate if timing requirements were met. We examined and reported the critical path of the one-digit BCD adder circuit and visually presented the timing waveforms associated with it.

Questions

1. Briefly explain your VHDL code implementation of all circuits.

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.NUMERIC_STD.ALL;
4
5 entity Karen_Chen_half_adder is
6 port(
7     a: in std_logic;
8     b: in std_logic;
9     s: out std_logic;
10    c: out std_logic);
11 end Karen_Chen_half_adder;
12
13 architecture structural of Karen_Chen_half_adder is
14 begin
15     process (a,b)
16     begin
17         s <= a xor b;
18         c <= (a and b);
19     end process;
20 end;
```

Figure 1. Structural description of half adder

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.NUMERIC_STD.ALL;
4
5 entity Karen_Chen_half_adder_tb is
6 --empty
7 end Karen_Chen_half_adder_tb;
8
9 architecture tb of Karen_Chen_half_adder_tb is
10
11     component Karen_Chen_half_adder
12     port(
13         a, b: in std_logic;
14         s, c: out std_logic);
15     end component;
16
17     signal a_in, b_in, s_out, c_out : std_logic;
18
19     begin
20         dut: Karen_Chen_half_adder port map(
21             a => a_in,
22             b => b_in,
23             c => c_out,
24             s => s_out);
25
26         test: process
27         begin
28             for i in std_logic range '0' to '1' loop
29                 a_in <= i;
30                 for j in std_logic range '0' to '1' loop
31                     b_in <= j;
32                     wait for 10 ns;
33                 end loop;
34             end loop;
35             wait;
36         end process;
37     end tb;
```

Figure 2. Testbench for structural description of half adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Karen_Chen_full_adder is
6  port(
7    a: in std_logic;
8    b: in std_logic;
9    c_in: in std_logic;
10   s: out std_logic;
11   c_out: out std_logic);
12 end Karen_Chen_full_adder;
13
14 architecture structural of Karen_Chen_full_adder is
15   component Karen_Chen_half_adder
16   port(
17     a, b: in std_logic;
18     s, c: out std_logic);
19   end component;
20   signal sum, c_HA1, c_HA2: std_logic;
21
22 begin
23   HA1: Karen_Chen_half_adder
24     port map(a, b, sum, c_HA1);
25
26   HA2: Karen_Chen_half_adder
27     port map(sum, c_in, s, c_HA2);
28
29   c_out <= c_HA1 or c_HA2;
30
31 end;
32
33
34
35

```

Figure 3. Structural description of full adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Karen_Chen_full_adder_tb is
6  --empty
7  end Karen_Chen_full_adder_tb;
8
9  architecture tb of Karen_Chen_full_adder_tb is
10
11   component Karen_Chen_full_adder
12   port(
13     a: in std_logic;
14     b: in std_logic;
15     c_in: in std_logic;
16     s: out std_logic;
17     c_out: out std_logic);
18   end component;
19
20   signal a_in, b_in, c_in_in, s_out, c_out_out: std_logic;
21
22 begin
23   dut: Karen_Chen_full_adder port map(
24     a => a_in,
25     b => b_in,
26     c_in => c_in_in,
27     c_out => c_out_out,
28     s => s_out);
29
30   test: process
31   begin
32     for i in std_logic_range '0' to '1' loop
33       a_in <= i;
34       for j in std_logic_range '0' to '1' loop
35         b_in <= j;
36         for k in std_logic_range '0' to '1' loop
37           c_in_in <= k;
38           wait for 10 ns;
39         end loop;
40       end loop;
41     end loop;
42     wait;
43   end process;
44
45 end tb;
46
47

```

Figure 4. Testbench for structural description of full adder

Figure 1 and 3 illustrate the structural descriptions for half adder and full adder respectively. The half adder takes two inputs and produces one sum and one carry out, in which the sum is generated by the XOR gate and carry out is produced by an AND gate. Whereas the full adder takes 2 inputs, 1 carry-in and produces 1 carry out and 1 sum. It implements 2 half adders and 1 OR gate. Figure 3 and 4 are the testbench codes that perform exhaustive tests for the structural descriptions.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.numeric_std.all;
4
5  entity Karen_Chen_rca_structural is
6  port(
7    A, B: in std_logic_vector (3 downto 0);
8    S: out std_logic_vector (4 downto 0)
9  );
10 end Karen_Chen_rca_structural;
11
12 architecture rca_struct of Karen_Chen_rca_structural is
13   -- use full adders in RCA
14   component Karen_Chen_full_adder
15   port(
16     a,b, c_in: in std_logic;
17     s,c_out: out std_logic);
18   end component;
19
20   -- carry/temporary variables
21   signal c_FA1, c_FA2, c_FA3: std_logic;
22
23 begin
24   -- order of mapping: a, b, c_in, s, c_out
25   -- pattern of mapping:
26   -- FA_i --> A(i), B(i), c_FA(i-1), S(i), c_FA(i)
27
28   -- Could have used a half_adder ;)
29   FA1: Karen_Chen_full_adder
30     port map(A(0), B(0), '0', S(0), c_FA1);
31   -- c_in of FA1 is '0'
32
33   FA2: Karen_Chen_full_adder
34     port map(A(1), B(1), c_FA1, S(1), c_FA2);
35
36   FA3: Karen_Chen_full_adder
37     port map(A(2), B(2), c_FA2, S(2), c_FA3);
38
39   FA4: Karen_Chen_full_adder
40     port map(A(3), B(3), c_FA3, S(3), S(4));
41 end;

```

Figure 5. Structural description of 4-bit Ripple-Carry-Adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.all;
3  use IEEE.numeric_std.all;
4
5  entity Karen_Chen_rca_structural_tb is
6  --empty
7  end Karen_Chen_rca_structural_tb;
8
9  -- Testbench for the half-adder
10 architecture tb of Karen_Chen_rca_structural_tb is
11   component Karen_Chen_rca_structural
12   port(
13     A, B: in std_logic_vector (3 downto 0);
14     S: out std_logic_vector (4 downto 0)
15   );
16   end component;
17
18   SIGNAL A_in, B_in: std_logic_vector (3 downto 0);
19   SIGNAL S_out: std_logic_vector (4 downto 0);
20
21 begin
22   -- device under test
23   DUT: Karen_Chen_rca_structural
24     port map(A_in, B_in, S_out);
25
26   Simuli: process
27   begin
28     report "STRUCTURAL RCA using 4 Full-Adders test";
29     for i in 0 to 15 loop --2^4(bit width)-1 = 15
30       A_in <= std_logic_vector(to_unsigned(i,4));
31       for j in 0 to 15 loop
32         B_in <= std_logic_vector(to_unsigned(j,4));
33         wait for 10 ns;
34       end loop;
35     end loop;
36     report "FINISHED!";
37     wait;
38   end process;
39 end;

```

Figure 6. Testbench for structural description of 4-bit RCA

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 --use ieee.std_logic_arith.all;
6 use ieee.std_logic_unsigned.all;
7
8 entity Karen_chen_rca_behavioral is
9 port(
10     A, B: in std_logic_vector (3 downto 0);
11     S: out std_logic_vector (4 downto 0)
12 );
13 end Karen_chen_rca_behavioral;
14
15 architecture rca_behave of Karen_chen_rca_behavioral is
16
17     --signal s_temp: std_logic_vector (4 downto 0);
18 begin
19     S<= '0' & A + B;
20 end;

```

Figure 7. Behavioral description of 4-bit Ripple-Carry-Adder

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity Karen_chen_rca_behavioral_tb is
6 --empty
7 end Karen_chen_rca_behavioral_tb;
8
9 -- Testbench for the half-adder
10 architecture tb of Karen_chen_rca_behavioral_tb is
11 component Karen_chen_rca_behavioral
12 port(
13     A, B: in std_logic_vector (3 downto 0);
14     S: out std_logic_vector (4 downto 0)
15 );
16 end component;
17
18 SIGNAL A_in, B_in: std_logic_vector (3 downto 0);
19 SIGNAL S_out: std_logic_vector (4 downto 0);
20
21 begin
22     -- device under test
23     DUT: Karen_chen_rca_behavioral
24     port map(A_in, B_in, S_out);
25
26     Simuli: process
27     begin
28         report "BEHAVIORAL RCA test";
29         for i in 0 to 15 loop --2^4(bit width)-1 = 15
30             A_in <= std_logic_vector(to_unsigned(i,4));
31             for j in 0 to 15 loop
32                 B_in <= std_logic_vector(to_unsigned(j,4));
33                 wait for 10 ns;
34             end loop;
35         end loop;
36         report "FINISHED!";
37         wait;
38     end process;
39 end;

```

Figure 8. Testbench for behavioral description of 4-bit RCA

Figure 5 is the structural description of 4-bit RCA in which it implements 4 full adders and describes the necessary signals that connect the ports. Figure 7 shows the implementation through operators such that the sum produced by the RCA has 5 bits by adding a '0' at the left-hand side of input A and then operate addition with the input B. Figure 6 and 8 illustrates the testbench code for the 4-bit Ripple Carry Adder.

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity Karen_chen_bcd_adder_structural is
6 port(
7     A, B: in std_logic_vector (3 downto 0);
8     S: out std_logic_vector (3 downto 0);
9     C: out std_logic;
10 );
11 end Karen_chen_bcd_adder_structural;
12
13 architecture bcd_struct of Karen_chen_bcd_adder_structural is
14 component Karen_chen_rca_structural
15 port(
16     A, B: in std_logic_vector (3 downto 0);
17     S: out std_logic_vector (4 downto 0)
18 );
19 end component;
20
21 -- Using a Half_adder and a Full_adder to implement a 2-bit adder
22 component Karen_chen_Half_Adder
23 port(
24     a,b: in std_logic;
25     s,c: out std_logic;
26 );
27 end component;
28
29 component Karen_chen_Full_Adder
30 port(
31     a,b, c_in: in std_logic;
32     s,c_out: out std_logic;
33 );
34 end component;
35
36 signal Z: std_logic_vector(4 downto 0);
37 signal HA_C, FA_C, C_temp: std_logic;
38
39 begin
40     -- mapping patterns:
41     -- A of BCD => A of RCA
42     -- B of BCD => B of RCA
43     -- Z => S of RCA
44     -- (A, B, Z)
45     RCA1: Karen_chen_rca_structural
46     port map(A, B, Z);
47
48     -- Detect if sum is > 9, yields MUX_input
49     -- Z(4) (the carry out) = true: s_temp > 15
50     -- 2 other conditions: 9 < s_temp < 16
51     C_temp <= Z(4) or (Z(3) and (Z(2) or Z(1)));
52
53     -- Two-bit adder, yields temporary variable S(1) and S(2)
54     HA: Karen_chen_Half_Adder -- map(a,b,s,c)
55     port map(C_temp, Z(1), S(1), HA_C);
56
57     FA: Karen_chen_Full_Adder -- map(a, b, c_in, s, c_out)
58     port map(C_temp, Z(2), HA_C, S(2), FA_C);
59
60     -- Getting S(3)
61     S(3) <= Z(3) xor FA_C;
62
63     -- Mapping the output
64     S(0) <= Z(0);
65     C <= C_temp;
66 end;

```

Figure 9. Structural description of a BCD Adder

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity Karen_chen_bcd_adder_structural_tb is
6 --empty
7 end Karen_chen_bcd_adder_structural_tb;
8
9 architecture tb of Karen_chen_bcd_adder_structural_tb is
10 component Karen_chen_bcd_adder_structural
11 port(
12     A, B: in std_logic_vector (3 downto 0);
13     S: out std_logic_vector (3 downto 0);
14     C: out std_logic;
15 );
16 end component;
17
18 -- Testing variables
19 signal A_in, B_in, S_out: std_logic_vector(3 downto 0);
20 signal C_out: std_logic;
21
22 begin
23     dut: Karen_chen_bcd_adder_structural
24     port map(A_in, B_in, S_out, C_out);
25
26     -- This is how the test should proceed:
27     -- (+) The BCD adder only adds numbers from 0 to 9
28     -- (+) If the input is greater than 9, the output should be don't care '-'
29     -- (+) Exhaustive test produces all possible inputs as well as all possible output
30
31     simulate: process
32     begin
33         report "STRUCTURAL One-digit BCD adder Exhaustive Test";
34         for i in 0 to 9 loop
35             A_in <= std_logic_vector(to_unsigned(i,4));
36             for j in 0 to 9 loop
37                 B_in <= std_logic_vector(to_unsigned(j,4));
38                 wait for 10 ns;
39             end loop;
40         end loop;
41         wait;
42     end process;

```

Figure 10. Testbench for structural description of

BCD Adder

Figure 9 demonstrates the structural description of a BCD Adder. In which it takes two 4-bit numbers into a 4-bit RCA component to produce intermediate results. Then operate separately with half adder and full adder in order to produce the final results: S_0 is same as intermediate result, Z_0 ; S_1 and S_2 are produced by a 2-bit RCA; S_3 is yield by a XOR gate with the intermediate Z_3 and carry out of the 2-bit CRA; finally the final carry out is produced by Z_4 OR (Z_2 OR Z_1)) as shown in line 49. Figure 10 illustrates the testbench for structural description of BCD adder.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity karen_chen_bcd_adder_behavioral is
7  port(
8    A, B: in std_logic_vector (3 downto 0);
9    S: out std_logic_vector (3 downto 0);
10   C: out std_logic);
11 end karen_chen_bcd_adder_behavioral;
12
13 architecture bcd_behave of karen_chen_bcd_adder_behavioral is
14   signal temp: std_logic_vector(4 downto 0);
15   signal dont_care: std_logic_vector(3 downto 0) := "----"; --dont care--
16
17 begin
18   process(A,B,temp)
19   begin
20     if (A > "1001" OR B > "1001") then
21       S <= dont_care;
22       C <= '-';
23     else
24       temp <= ('0' & A) + B;
25       if temp < "01010" then
26         S <= temp(3 downto 0);
27         C <= '0';
28       else
29         S <= temp(4 downto 1);
30         C <= temp(0);
31       end if;
32     end if;
33   end process;
34 end;

```

Figure 11. Behavioral description of BCD Adder

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity karen_chen_bcd_adder_behavioral_tb is
6  --empty
7  end karen_chen_bcd_adder_behavioral_tb;
8
9  architecture tb of karen_chen_bcd_adder_behavioral_tb is
10   component karen_chen_bcd_adder_behavioral
11   port(
12     A, B: in std_logic_vector (3 downto 0);
13     S: out std_logic_vector (3 downto 0);
14     C: out std_logic);
15   end component;
16
17   -- Testing variables
18   signal A_in, B_in, S_out: std_logic_vector(3 downto 0);
19   signal C_out: std_logic;
20
21   begin
22     dut: karen_chen_bcd_adder_behavioral
23     port map(A_in, B_in, S_out, C_out);
24
25   simulate: process
26   begin
27     report "BEHAVIORAL One-digit BCD adder Exhaustive Test";
28     for i in 0 to 15 loop
29       A_in <= std_logic_vector(to_unsigned(i,4));
30       for j in 0 to 15 loop
31         B_in <= std_logic_vector(to_unsigned(j,4));
32         wait for 10 ns;
33       end loop;
34     end loop;
35     wait;
36   end process;
37 end;

```

Figure 12. Testbench for behavioral description of BCD Adder

Figure 11 demonstrates the behavioral architecture of BCD Adder, in which check whether the addition requires to add 00110, 6 in decimal, in order to convert binary number to BCD if it is greater than 9. Figure 12 is the testbench code that perform exhaustive tests for validating BCD adder.

2. Show representative simulation plots of the half-adder circuit for all possible input values.

 


Figure 13. Simulation of exhaustive tests of half adder

 


Figure 14. Schematic view of half adder

3. Show representative simulation plots of the full-adder circuit for all possible input values.

 


Figure 15. Simulation of exhaustive tests of full adder

 


Figure 16. Schematic view of full adder

4. Show representative simulation plots of both behavioral and structural descriptions of the 4-bit RCA for all possible input values.

 


Figure 17. Simulation of exhaustive tests of structural description of RCA

 


Figure 18. Simulation of exhaustive tests of RCA (Zoom-in ver.)

 


Figure 19. Schematic view of structural description of RCA



Figure 20. Simulation of exhaustive tests of behavioral description of RCA

 


Figure 21. Simulation of exhaustive tests of behavioral description of RCA (Zoom-in ver.)

 


Figure 22. Schematic view of behavioral description of RCA

5. Show representative simulation plots of both behavioral and structural descriptions of the one-digit BCD adder circuit for all possible input values.

 


Figure 23. Simulation of exhaustive tests of structural description of one-digit BCD



Figure 24. Simulation of exhaustive tests of structural description of one-digit BCD (Zoom-in ver.)

 


Figure 28. Schematic view of behavioral description of one-digit BCD

- Perform timing analysis and find the critical path(s) of the one-digit BCD adder circuit for the Fast 1,100 mV 85C Model. Show the obtained timing waveform(s) of the critical path(s) that you found.

 


Figure 29. Timing waveform of the critical path in one-digit BCD

Fast 1100mV 85C Model								
Command Info		Summary of Paths						
	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1	-0.602	A[1]	S[1]	A[1]	n/a	5.000	0.000	5.602
2	-0.275	B[0]	S[1]	n/a	n/a	5.000	0.000	5.275
3	-0.228	A[1]	S[3]	A[1]	n/a	5.000	0.000	5.228
4	-0.188	A[1]	S[2]	A[1]	n/a	5.000	0.000	5.188
5	-0.146	A[1]	S[3]	A[1]	n/a	5.000	0.000	5.146
6	-0.130	A[1]	S[2]	A[1]	n/a	5.000	0.000	5.130
7	-0.120	B[1]	S[1]	n/a	n/a	5.000	0.000	5.120
8	-0.112	A[1]	S[3]	A[1]	n/a	5.000	0.000	5.112
9	-0.003	A[1]	S[1]	A[1]	n/a	5.000	0.000	5.003
10	0.103	A[0]	S[1]	n/a	n/a	5.000	0.000	4.897
11	0.166	B[0]	S[2]	n/a	n/a	5.000	0.000	4.834
12	0.180	B[0]	S[3]	n/a	n/a	5.000	0.000	4.820
13	0.227	B[0]	S[3]	n/a	n/a	5.000	0.000	4.773
14	0.249	B[0]	S[0]	n/a	n/a	5.000	0.000	4.751
15	0.267	B[0]	S[2]	n/a	n/a	5.000	0.000	4.733
16	0.287	A[3]	S[3]	n/a	n/a	5.000	0.000	4.686
17	0.314	B[3]	S[3]	n/a	n/a	5.000	0.000	4.686
18	0.317	A[2]	S[3]	n/a	n/a	5.000	0.000	4.683
19	0.318	B[1]	S[2]	n/a	n/a	5.000	0.000	4.682
20	0.323	B[1]	S[3]	n/a	n/a	5.000	0.000	4.677
21	0.332	B[1]	S[3]	n/a	n/a	5.000	0.000	4.668
22	0.343	B[0]	S[3]	n/a	n/a	5.000	0.000	4.657
23	0.357	A[2]	S[2]	n/a	n/a	5.000	0.000	4.643
24	0.363	B[1]	S[2]	n/a	n/a	5.000	0.000	4.637
25	0.366	A[1]	S[3]	A[1]	n/a	5.000	0.000	4.634
26	0.375	B[2]	S[3]	n/a	n/a	5.000	0.000	4.625
27	0.380	B[2]	S[3]	n/a	n/a	5.000	0.000	4.620
28	0.380	A[2]	S[3]	n/a	n/a	5.000	0.000	4.620
29	0.399	B[2]	S[2]	n/a	n/a	5.000	0.000	4.601
30	0.408	A[1]	S[2]	A[1]	n/a	5.000	0.000	4.592
31	0.439	B[1]	S[3]	n/a	n/a	5.000	0.000	4.561
32	0.453	A[1]	S[3]	A[1]	n/a	5.000	0.000	4.547
33	0.469	A[1]	S[2]	A[1]	n/a	5.000	0.000	4.531
34	0.475	A[1]	S[3]	A[1]	n/a	5.000	0.000	4.525
35	0.544	A[0]	S[2]	n/a	n/a	5.000	0.000	4.456
36	0.558	A[0]	S[3]	n/a	n/a	5.000	0.000	4.442
37	0.581	A[0]	S[0]	n/a	n/a	5.000	0.000	4.419
38	0.605	A[0]	S[3]	n/a	n/a	5.000	0.000	4.395
39	0.645	A[0]	S[2]	n/a	n/a	5.000	0.000	4.355
40	0.721	A[0]	S[3]	n/a	n/a	5.000	0.000	4.279

Figure 30. Summary of paths of the critical path in one-digit BCD

- Report the number of pins and logic modules used to fit your designs on the FPGA board.

	RCA		One-digit BCD adder	
	Structural	Behavioral	Structural	Behavioral
Logic Utilization(in LUTs)	4/32070 (<1%)	3/32070 (<1%)	7/32070 (<1%)	9/32070 (<1%)
Total pins	13/457 (3%)	13/457 (3%)	13/457 (3%)	13/457 (3%)

Explanations of the Results

In Figure 13, the simulation plots for the Half-Adder circuit offer a comprehensive insight into its fundamental operation. They encompass a range of input combinations, including both '0' and '1' states for inputs A and B, which are essential to demonstrate the circuit's binary addition functionality. The Sum (S) output should correctly reflect the result of adding A and B, showing '1' when A and B are different and '0' when they are the same. The Carry (C) output should indicate the generation of a carry only when both A and B are '1.' The plots also reveal transition times and propagation delays, which are critical for assessing the circuit's speed. Consistency across all simulations is essential to confirm that the circuit operates as expected for all possible input combinations, aligning with the logical rules of binary addition. Additionally, when comparing simulation plots of both structural and behavioral implementations, any discrepancies or differences would highlight design issues, emphasizing the importance of correctness and equivalency in the designs.

In the Figure 15 which is simulation plots for a full-adder circuit, the waveforms of the input signals (A, B, and Cin) should accurately represent various combinations of binary inputs transitioning between logic levels '0' and '1.' These plots should demonstrate the full-adder's ability to add three inputs, including an optional carry-in (Cin). The output signals, Sum (S) and Carry-out (Cout), should exhibit their expected behavior. Specifically, when all inputs are '0,' both Sum and Cout should be '0,' indicating no carry and a sum of '0.' When appropriate inputs are '1,' the Sum should reflect the binary sum, while Cout should indicate the presence or absence of carry. For example, When A is '1', B is '0' and Cin is '0', the Sum should be '1', and Cout should be '0', as there is no carry. The simulation plots should comprehensively test different input scenarios, ensuring that the full-adder adheres to binary addition rules and correctly handles carry propagation and generation.

In Figure 17 which is the simulation plots for the 4-bit Ripple-Carry Adder (RCA), both the structural and behavioral implementations should exhibit the expected behavior of an adder circuit. The waveforms of the input signals (A and B) should reflect various combinations of 4-bit binary inputs transitioning between logic levels '0' and '1.' These plots should effectively demonstrate the functionality of the 4-bit RCA, showcasing its ability to perform binary addition on multi-bit inputs. The Sum (S) output should represent the accurate sum of the inputs, adhering to binary addition rules. The Carry-out (Cout) signal should show the generation of carry when required. By comparing the results of the structural and behavioral implementations, the simulation plots should illustrate that both approaches yield the same correct output, emphasizing the functional equivalence of the two designs. This comprehensive testing ensures that the 4-bit RCA correctly handles carry propagation and generation across multiple bits, a fundamental aspect of arithmetic circuits.

In Figure 26, which is the simulation plots for the One-Digit BCD Adder (Structural and Behavioral) provide valuable insights into the functionality of this circuit. In the context of structural implementation, these plots illustrate the interconnection of basic logic components, demonstrating how the BCD Adder processes input data and produces output results. The simulation plots should confirm that the structural implementation adheres to the logical

principles of binary-coded decimal addition. They should show the formation of the correct BCD digits for each sum and the generation of a carry when the sum exceeds '9' in BCD format.

Conclusions

Through this experiment, we learned how to:

- Use Quartus Timing Analyzer tools to find the critical path.
- Create VHDL descriptions and testbenches for a ripple-carry in behavioral and structural styles through practice with Half Adder and Full Adder.
- Create VHDL descriptions and testbenches for BCD adders including behavioral and structural styles.
- Enhance our observations and comprehensions on the architecture sections through the debugging process and RTL simulation analysis.